STAIRCASE WIRING:

CIRCUIT DIAGRAM:

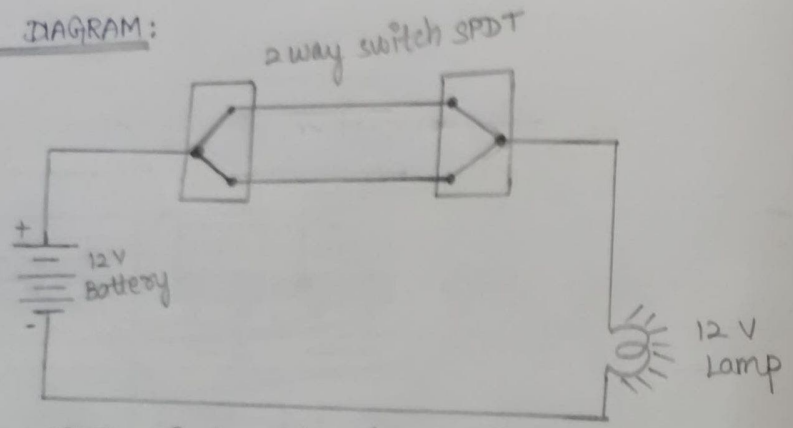

SPDT - single pole double throw switch

Mode	S_1	S_2	Lamp
1	ON	ON	ON
2	ON	OFF	OFF
3	OFF	ON	OFF
4	OFF	OFF	ON

Components	Proteus	Specification
AC supply	V sine	Amplitude 230V
Two-way switch	SPDT	Frequency 50Hz
Lamp	Animated	230V

Expt. No. 03

Page No. 10

DATE: 23/09/26

STAIRCASE WIRING

AIM:

To develop and test the staircase wiring using proteus.

APPARATUS REQUIRED:

Laptop with proteus software

THEORY:

Staircase wiring is a common multiple way switching or two way switching connection. It involves wiring for one light with two switches. In this set up is controlled by two switches located operates the load from seperates position above or below the staircase from inside or outside of room or two way led switch.

PROCEDURE:

* Drag the required components from the process library.

Cross connection

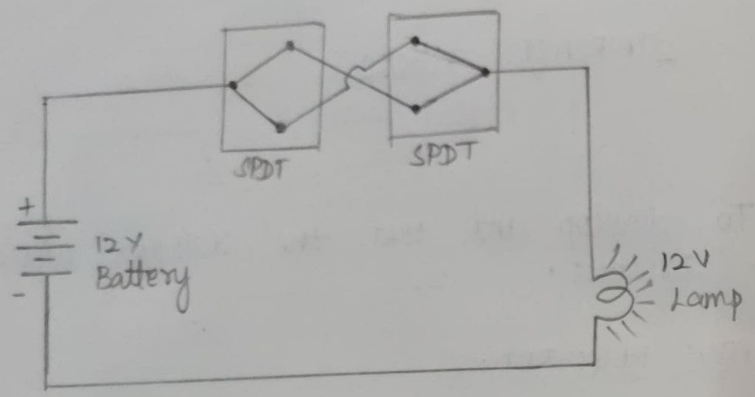

Mode	S_1	S_2	Lamp
1.	ON	ON	OFF
2.	ON	OFF	ON
3.	OFF	ON	ON
4.	OFF	OFF	OFF

* Connect the components as per circuit diagram.

* Run the simulation and check the lamp for different switching condition.

99

02/03/2026

RESULT:

Thus the staircase using connection were developed and tested successfully.

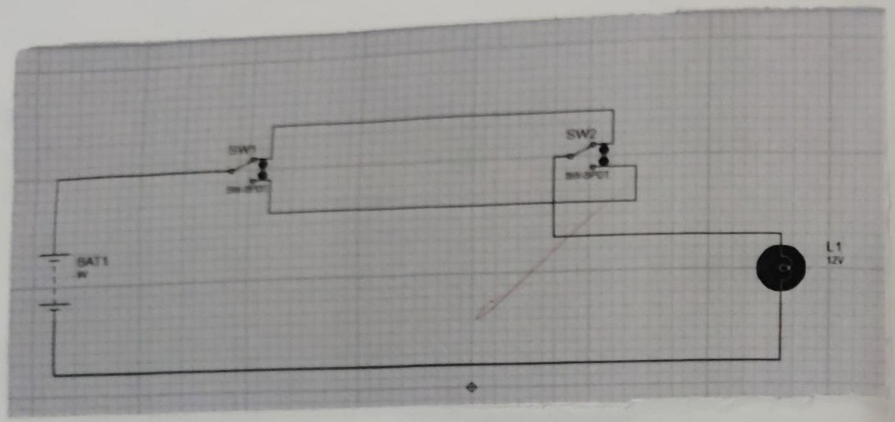
SW1
SW2
SW-SPDT
SW-SPDT
BAT1
9V
L1
12V

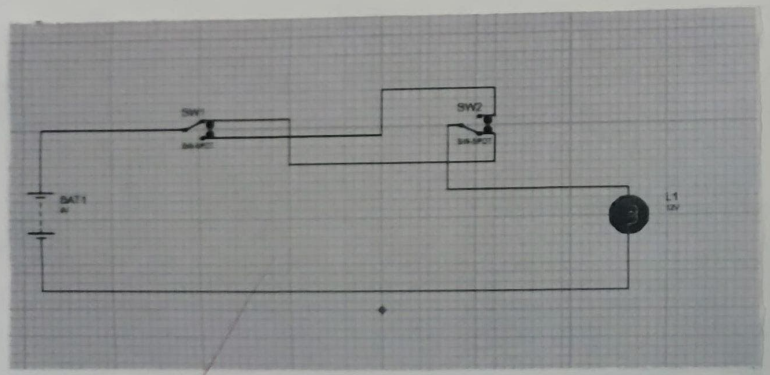
SW1
SW2
SW-SPDT
SW-SPDT
BAT1
9V
L1
12V